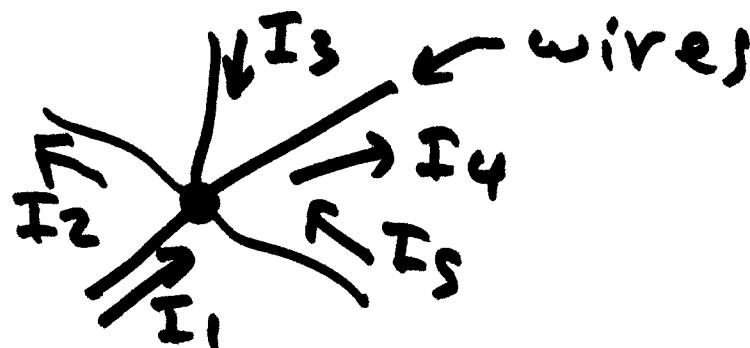


# Kirchhoff's laws

1-9-02

(6)

## 1) Kirchhoff's current law (KCL)



The total current entering the node is equal to the total current leaving the node

Assign + for entering current  
- for leaving

$$+I_1 + I_5 + I_3 \quad \left. \begin{array}{l} | \\ I_1 + I_5 + I_3 = \\ | I_2 + I_4 | \end{array} \right\} -I_2 - I_4$$

$$\sum = 0$$

currents


$$\Rightarrow I_1 + I_5 + I_3 - I_2 - I_4 = 0$$

$$I_1 + I_5 + I_3 = I_2 + I_4$$

(7)

KCL  $\sum_{\text{all } k} i_k = 0$  At a node

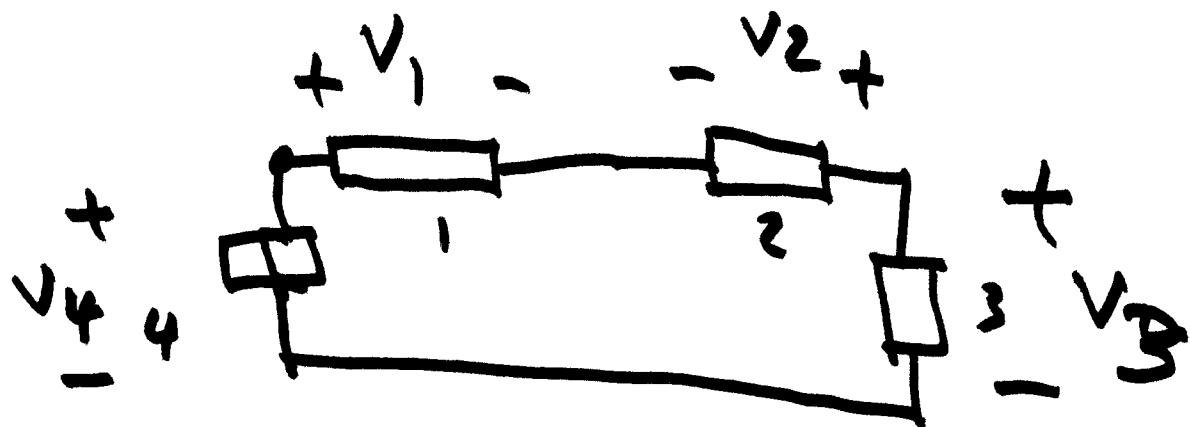2) Kirchoff's Voltage law (KVL)  
closed Path.



KVL: Algebraic summation  
of voltages around  
a closed Path is zero

$$+V_1 - V_2 + V_3 - V_4 = 0$$


generalize

KVL:  $\sum_{\text{all } k} V_k = 0$  around a  
closed Path

## Other circuit elements



(8)

### Ideal voltage source

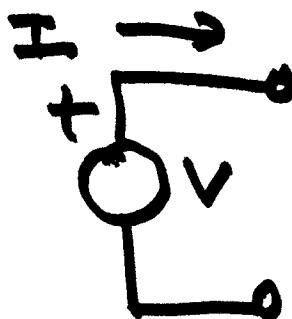

maintains voltage  $V$   
across its terminals  
independent of  $I$


OR

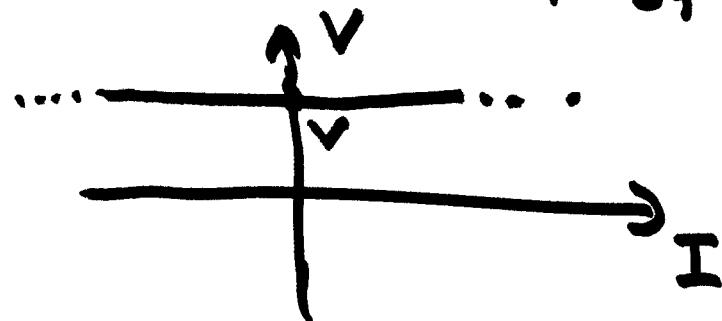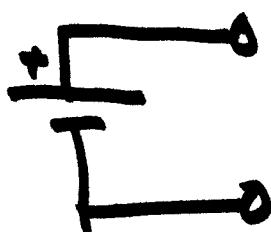

V-I characteristic

Ideal voltages are useful in:-

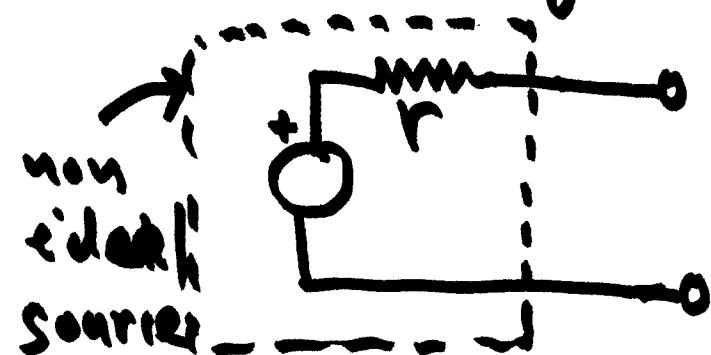
- 1) College and Engineering of Theory
- 2) Modeling non-ideal (Practical) voltage sources



r: internal  
Resistance


(9)

# Ideal current source

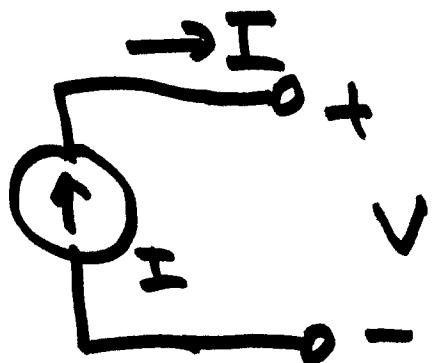

maintains current

$I$ , independent  
of voltage

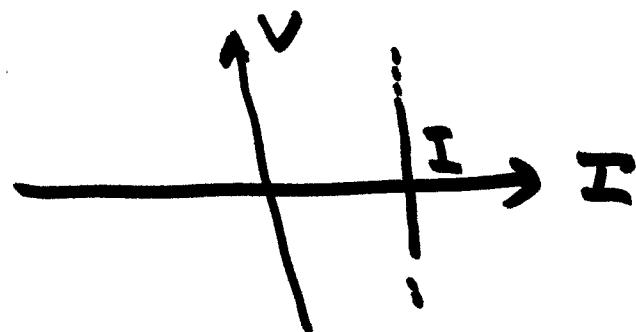


useful in:  
1) college  
2) TBA

Back to circuits using  
Resistors and DC sources

Example (1)

$$I = I_1 \text{ (FCL)}$$

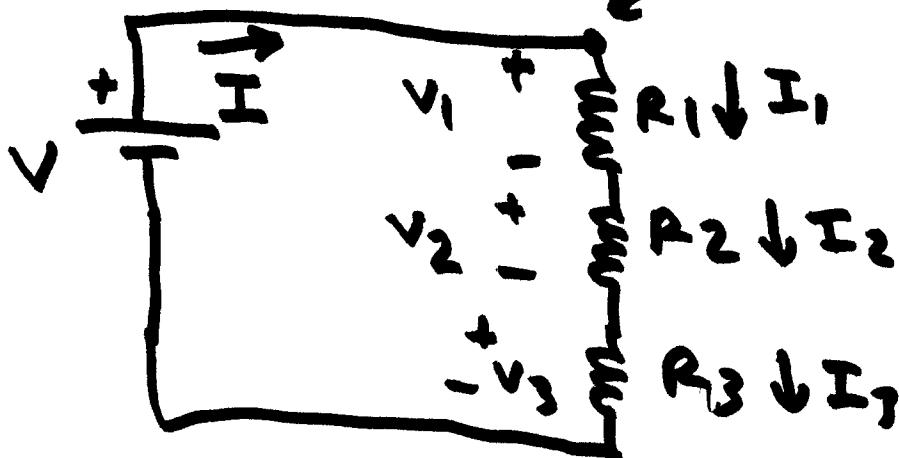

## Circuit analysis:-

compute voltage and current of each component in the circuit

In the example:-

$$\text{KCL. } I_1 = I_2 = I_3 = I \text{ (A)}$$

$$\text{KVL } +V_1 + V_2 + V_3 - V = 0$$

$$\Rightarrow V = V_1 + V_2 + V_3 \text{ (B)}$$

$$\text{By Ohm's Law } V_1 = I_1 R_1$$

$$V_2 = I_2 R_2$$

$$V_3 = I_3 R_3$$

$$(B) \Rightarrow V = \underbrace{I_1 R_1}_{V_1} + \underbrace{I_2 R_2}_{V_2} + \underbrace{I_3 R_3}_{V_3}$$

$$\rightarrow V = I (R_1 + R_2 + R_3) \text{ (C)}$$

$$\Rightarrow I = \frac{V}{R_1 + R_2 + R_3}$$

(ii)  $I = I_1 = I_2 = I_3$  (Resistor currents)

Find Resistor Voltages

From Ohm's Law

$$V_1 = I_1 R_1 = V \cdot \frac{R_1}{R_1 + R_2 + R_3}$$

$$V_2 = V \cdot \frac{R_2}{R_1 + R_2 + R_3}$$

$$V_3 = V \cdot \frac{R_3}{R_1 + R_2 + R_3}$$

Numerical example

$$V = 12V \quad R_1 = R_2 = R_3 = 4\Omega$$

$$\Rightarrow I = \frac{12}{4+4+4} = 1A$$

$$V_1 = 4V$$

$$V_2 = 4V$$


$$V_3 = 4V$$

## Special case

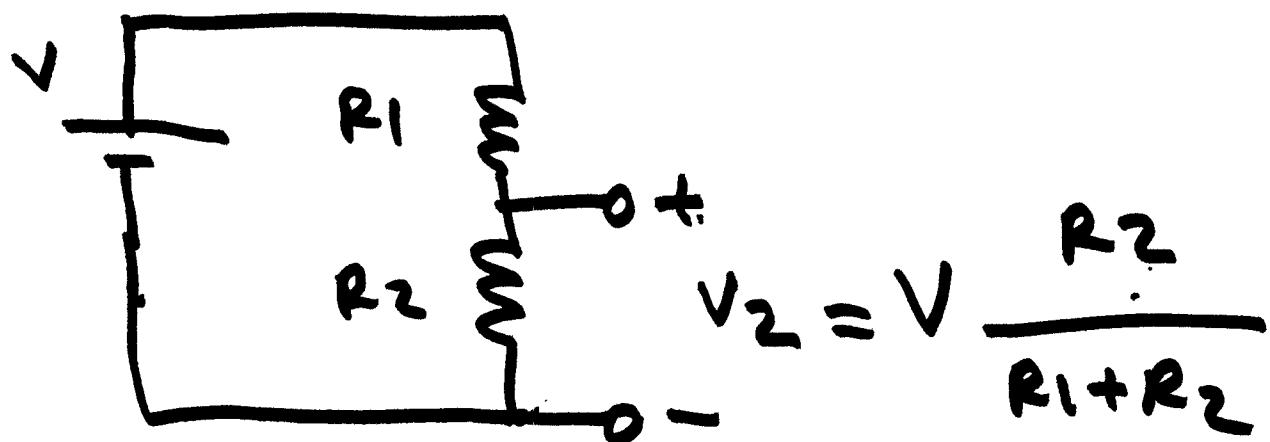(12)


Same circuit as in example  
with only 2 resistors  
(make  $R_3 = 0 \Omega$ )

$$I = \frac{V}{R_1 + R_2}, V_1 = V \frac{R_1}{R_1 + R_2}, V_2 = V \frac{R_2}{R_1 + R_2}$$




Voltage divider  
rule

How about  $V_1$

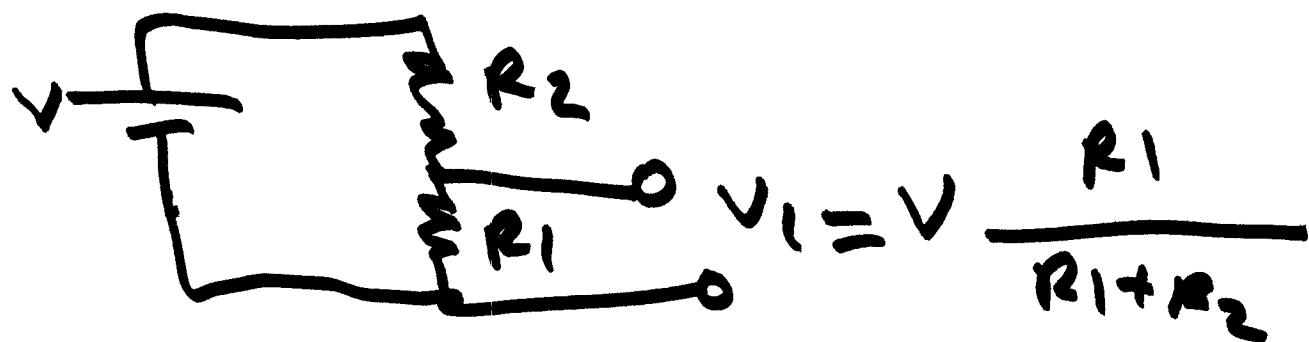

# measurements

measure voltage

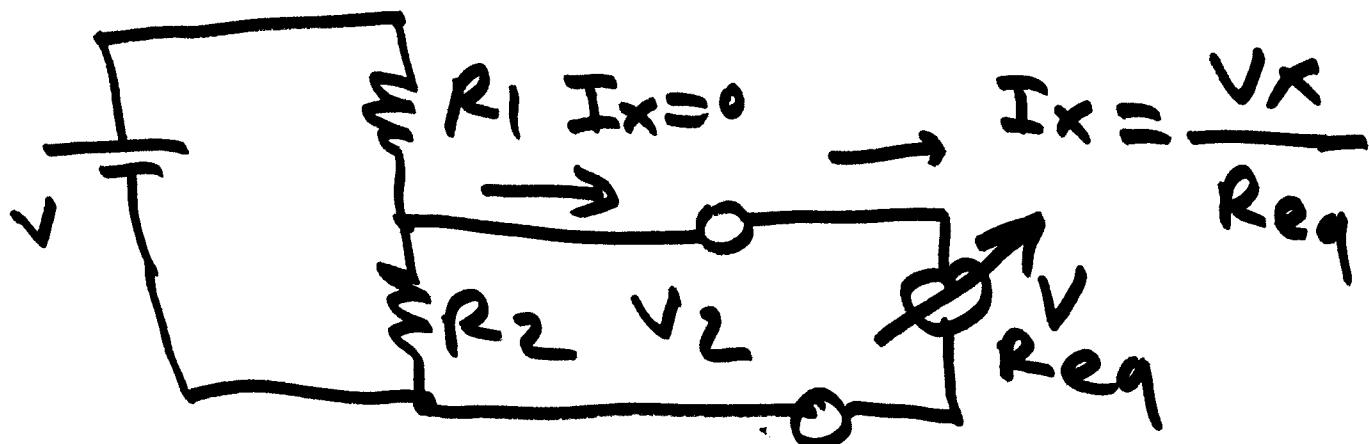


$$V_2 = V \frac{R_2}{R_1 + R_2}$$

$$\Rightarrow R_{eq} \rightarrow \infty$$

# Connections of resistors

#  
⑯

## 1) Series connection

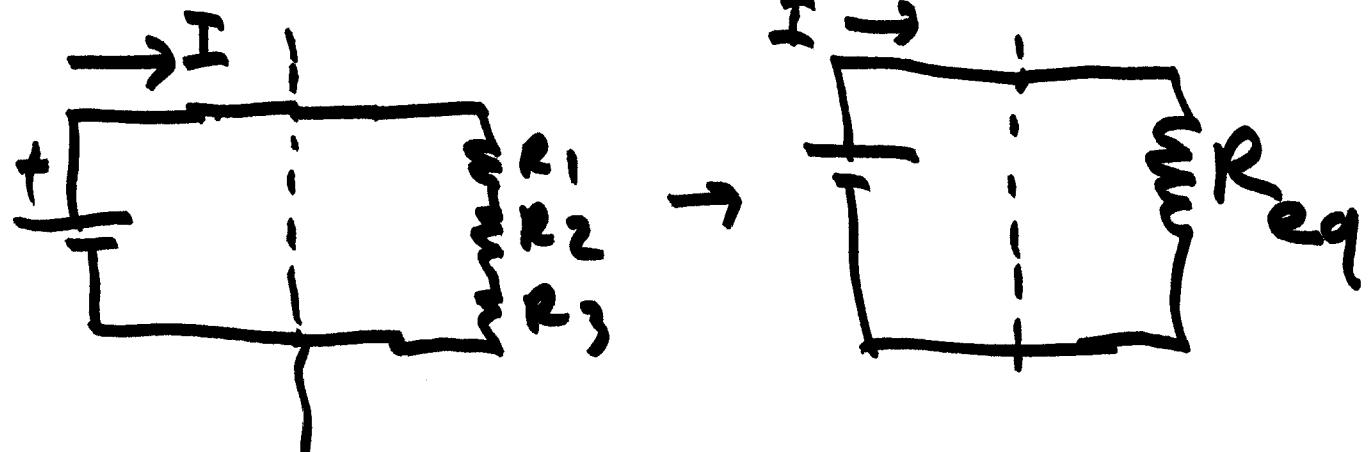

$Req$  has the same effect  
as  $R_1, R_2, R_3$  ??

$$I = \frac{V}{R_1 + R_2 + R_3}$$

(Actual circuit)

actual circuit

$$I = \frac{V}{Req}$$

(Equivalent)

equivalent

$$\Rightarrow Req = R_1 + R_2 + R_3$$

Generalize: -  $N$ , Resistor in series,

$$Req = R_1 + R_2 + \dots + R_N = \sum_{i=1}^N R_i$$