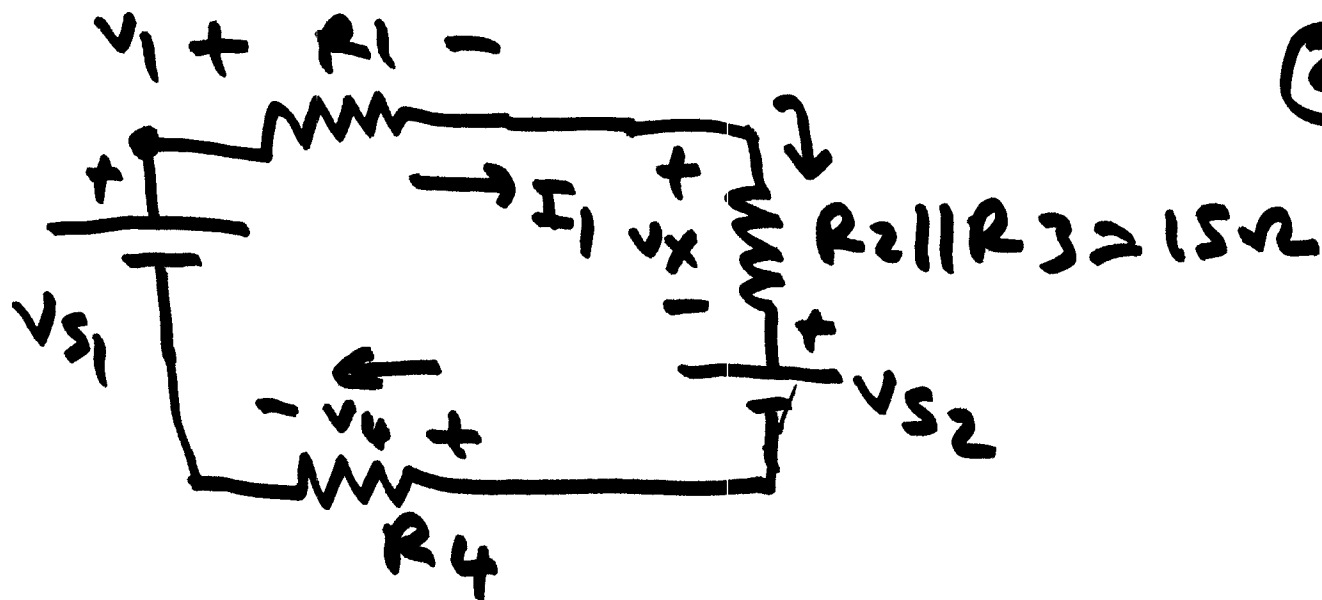


(24)



$$\text{KVL: } +V_1 + V_x + V_{S2} + V_4 - V_{S1} = 0$$

$$I_1 \cdot R_1 + I_1 R_2 \parallel R_3 + V_{S2} + I_1 R_4 - V_{S1} = 0$$

$$I_1 [R_1 + R_2 \parallel R_3 + R_4] = V_{S1} - V_{S2}$$

$$I_1 = \frac{V_{S1} - V_{S2}}{[10 + 15 + 30]} = \frac{120 - 65}{55} = 1 \text{ A}$$

Compute  $I_2, I_3$

$$I_2 = I_1 \cdot \frac{R_3}{R_2 + R_3}, \quad I_3 = I_1 \cdot \frac{R_2}{R_2 + R_3}$$


$$I_2 = \frac{3}{4} \text{ A} //$$

$$I_3 = \frac{1}{4} \text{ A} //$$

# Power in Resistors

1-16-02

(25)

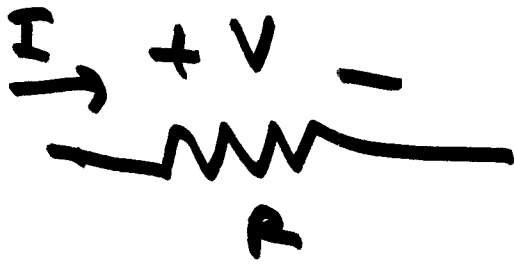

Power:  $P = V \cdot I$  Since  $I = \frac{V}{R}$

$$\Rightarrow P = \frac{V^2}{R} = I^2 R \text{ (W)}$$

$$\text{Energy} = \int_{t_1}^{t_2} P(t) dt$$

$$= P \cdot (t_2 - t_1) \text{ if}$$

$$P = \text{constant}$$


Electrical energy is usually measured by

Power companies in kWh

Conservation of energy (or power)  
(input energy) = (output energy)

Power from voltage  
Source)

26

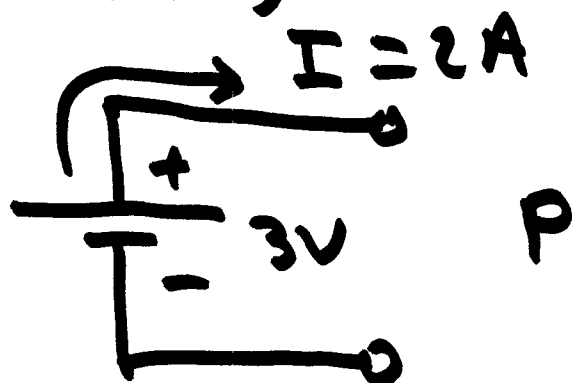


A voltage source  
delivers power to  
the outside world  
if the current flows  
out of the (+) terminal

Agreement: we will  
call power delivered from  
a source positive.

Example: Prob 1.19

27

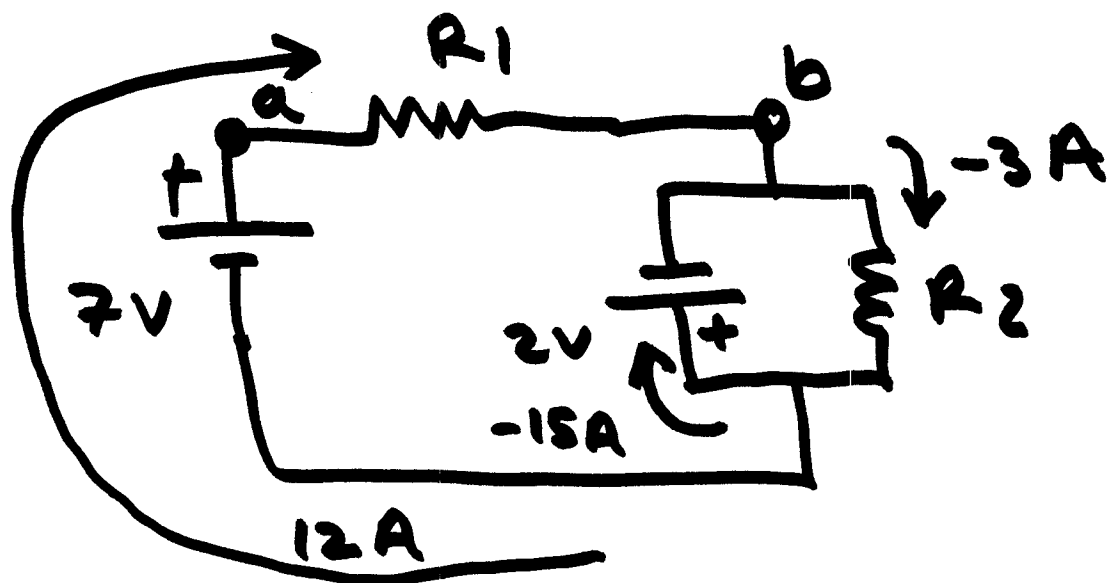

$$V_{ab} = 9V$$

$$P_{R_1} = V_{R_1} \cdot I_{R_1} = V_{ab} \times 12A \\ = 9V \times 12A = 108W$$

$$P_{R_2} = -I_{R_2} \cdot 2V$$

$$P_{R_2} = -(-3) \cdot 2 = 6W$$

$$P_{R_2} = -(-3) \cdot 2 = 6W$$

2V source

$$P = 2V \times 15A = 30W$$

$$|P| = 2V \times 15A \\ = 30W$$

Actually

$$P_{\text{delivered}} = -VI = -(-15) \times 2 \\ = 30 \text{ W}$$

The 30W is delivered  
to the circuit

Power from 7V source

$$I_2 \uparrow \frac{1}{T}^+ 7V$$

$$P_{\text{delivered}} = I_2 \cdot 7V \\ = 7 \times 12V = 84 \text{ W}$$

$$\left. \begin{array}{l} \text{Power delivered} \\ \text{to circuit} \end{array} \right\} P_{7V} + P_{2V} \\ 84 + 30 = 114 \text{ W}$$

$$\text{Power lost} = P_{R1} + P_{R2} = 108 \text{ W} + 6 \text{ W}$$

(29)

Power delivered = 114 W

Power lost = 114 W


---

Connections of Sources

a) voltage sources

1) series connection

voltages add algebraically

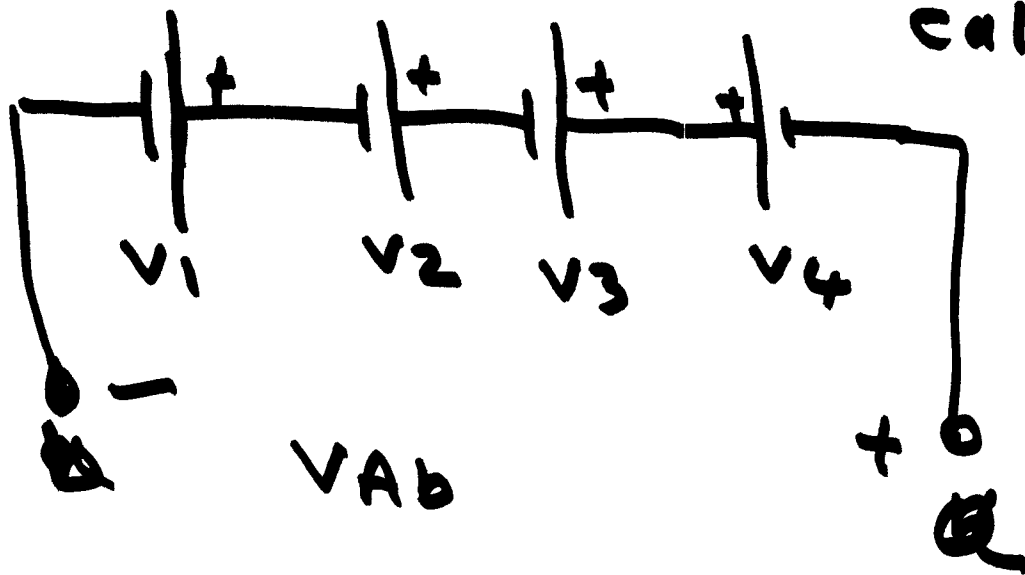


$$V_{AB} - V_1 - V_2 - V_3 + V_4 = 0$$

$$V_{AB} = V_1 + V_2 + V_3 - V_4$$

2) Parallel

30

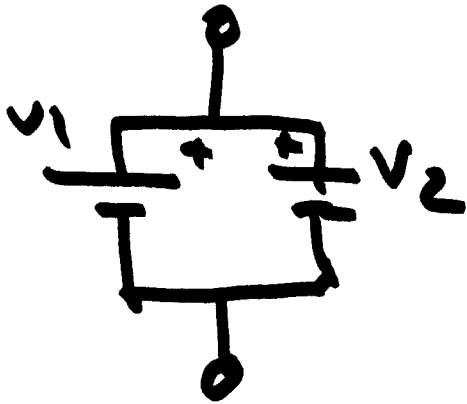

SOS!!

when connecting  
voltage sources  
in parallel


they MUST have

the same voltage, otherwise  
they will explode


## b) Current Source

(31)

### 1) Parallel

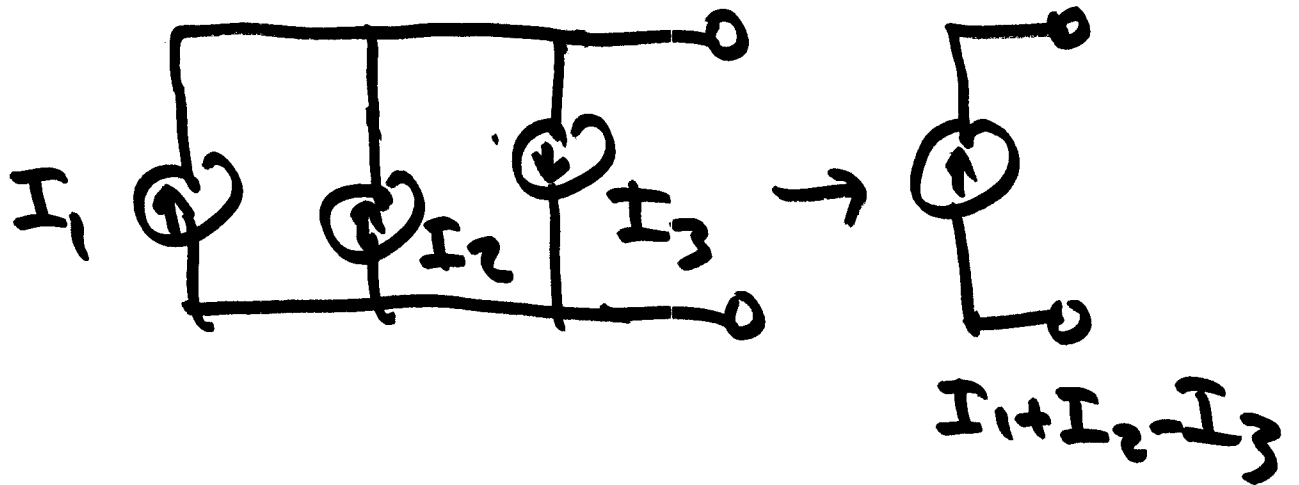

### 2) Series Connection

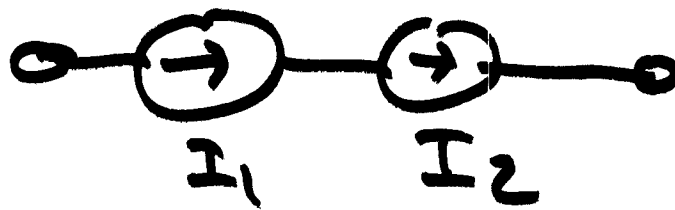


~~///~~  $I_1$  must be equal to  $I_2$



# Equivalent (Internal) Resistance of Source

## A) Voltage Source


Non-ideal Source

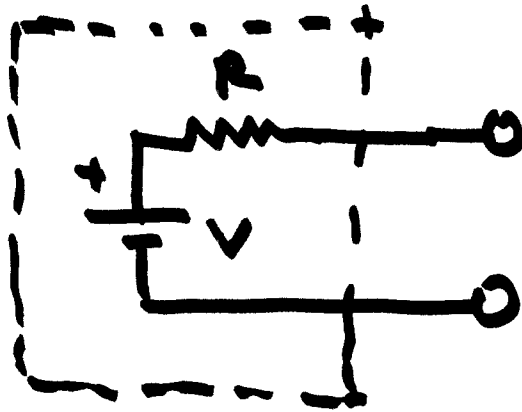

measure  $R$

1) measure open-circuit voltage.  $V_{oc} = V$

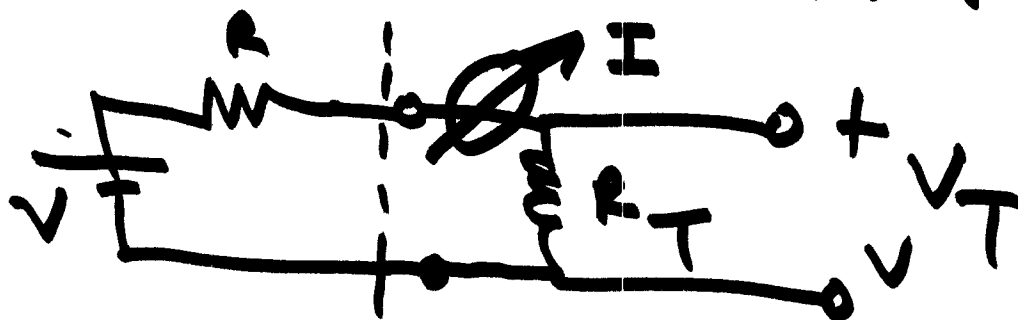2) Connect a test Resistor at it's terminals



Apply voltage divider

$$V_T = V - I \cdot R$$

$\uparrow$  known       $\uparrow$   $V_{OC}$  known       $\uparrow$  known

$$R = \frac{V - V_T}{I - 0} = \frac{\Delta V}{\Delta I}$$

$$\Rightarrow R = \frac{\Delta V}{\Delta I}$$

$$V_T = V \cdot \frac{R_T}{R_T + R}$$

$\uparrow$  measured       $\uparrow$  known       $\uparrow$  solve

---

Return  $R = \frac{\Delta V}{\Delta I}$

In ideal source

34

$$\Delta V = 0 \Rightarrow R = 0$$

when  $V$  becomes  
Zero, the ideal voltage  
source looks like a  
short circuit

