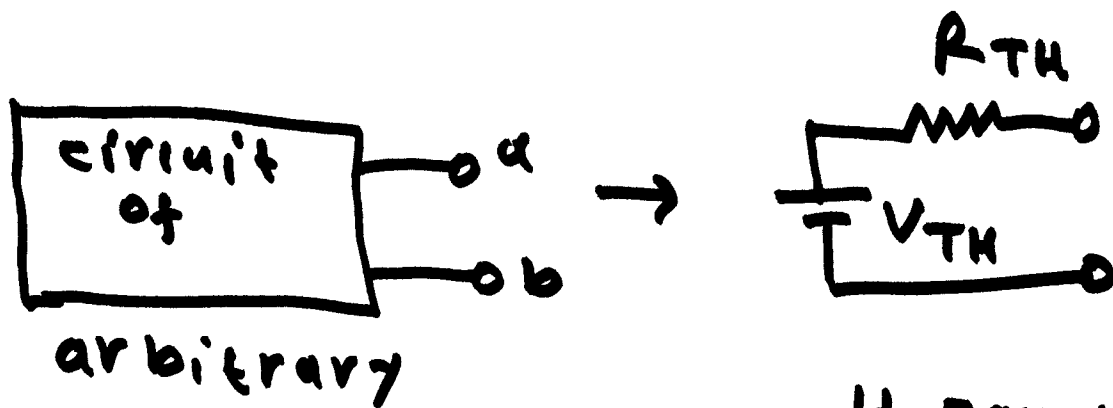


Thevenin's Theorem

(49)

1/28/02




Complexity
Assume that
it contains
Resistors and
independent
source(s)

Assume that
it does not
contain
non-linear
components

It can be
reduced to
a voltage
source with
a resistor
in series

Obtain V_{TH} , R_{TH}

Let

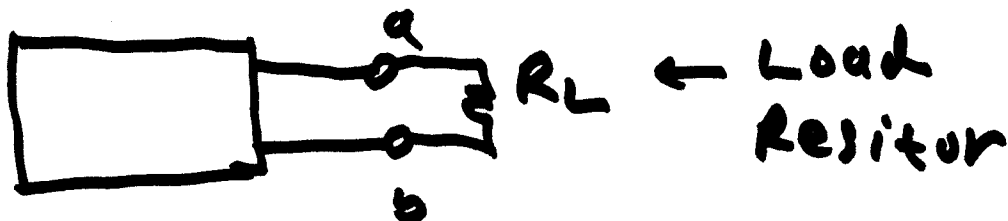


Find Thevenin equivalent
as seen by R_L .

(50)

Step 1 Remove R_L

Step 2 V_{TH} : open circuit voltage
between points a b

$$V_{TH} = V_{ab} \big|_{\text{open circuit}}$$

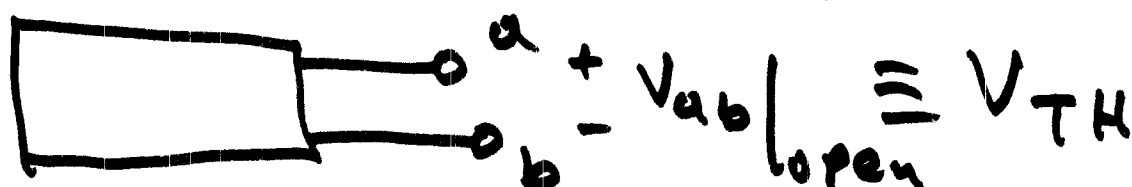


Step 3 Compute R_{TH}


a) Set all independent sources
to zero

Note zero voltage \rightarrow short
zero current \rightarrow open

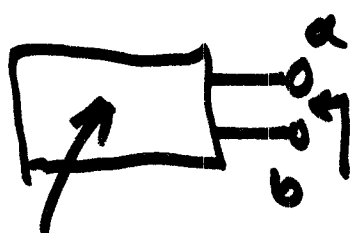b) Compute the equivalent
resistance between
points a b




$$\text{sources} = 0 \quad R_{eq,a,b} \quad R_{TH} \equiv R_{eq,a,b} \big|_{\text{sources} = 0}$$

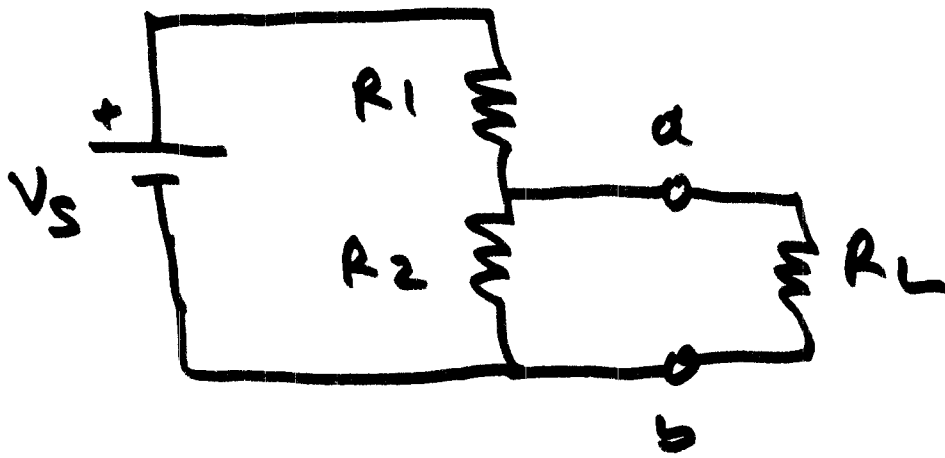Example

Find the Thevenin equivalent
between points a, b, as seen
by R_L

1) Remove R_L

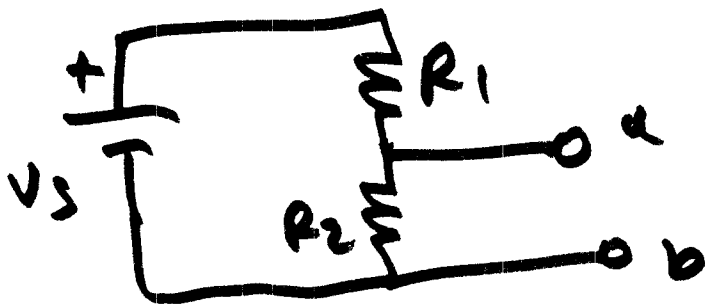


$$V_{ab} = V_{TH}$$

→ Voltage divider:
step 2


$$V_{ab} = V_{TH} = V_S \frac{R_2}{R_1 + R_2}$$

step 3 set $V_S = 0$

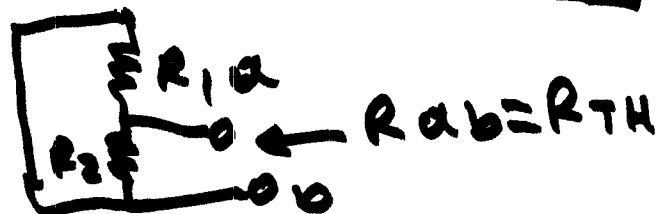


Another example

(53)

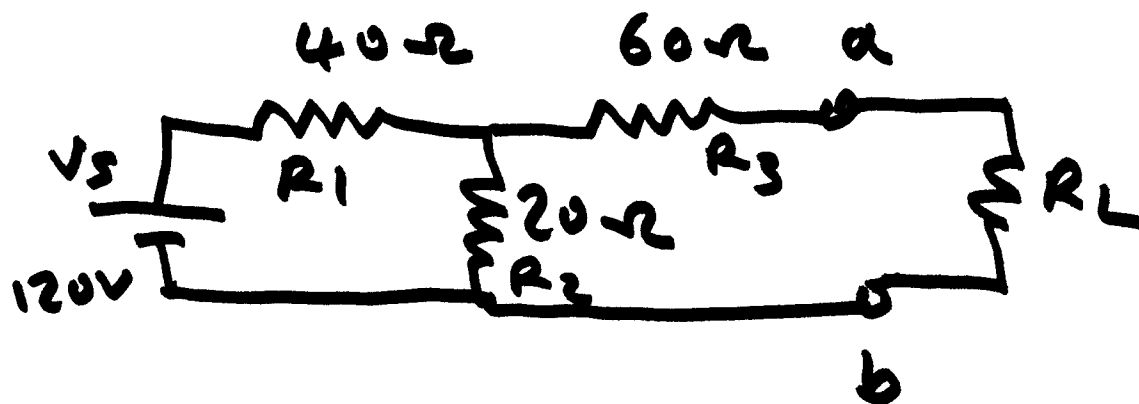

Find thevenin seen by R_L

Step 1) Remove R_L

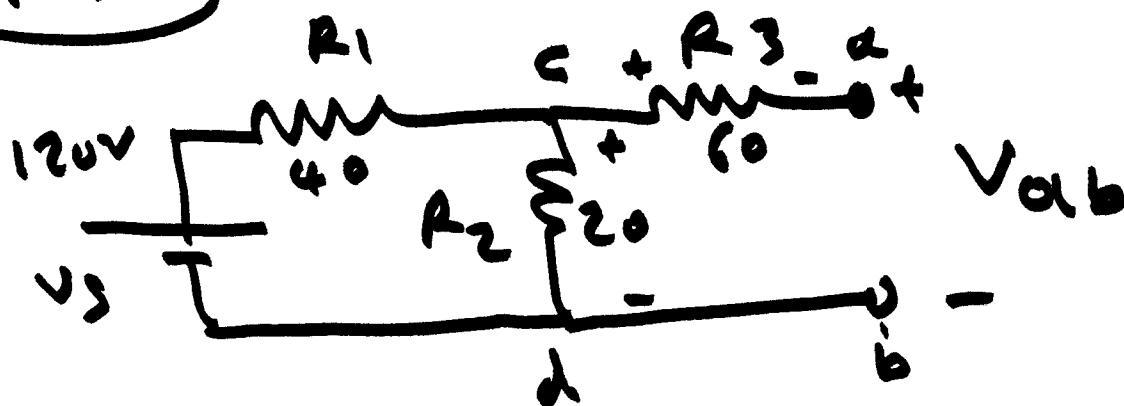

$$V_{cd} = V_s \frac{R_2}{R_1 + R_2}$$

$$\text{KVL: } V_{ca} + V_{ab} - V_{dc} = 0$$


$$\Rightarrow V_{ab} = +V_{dc} = V_{ca}$$

$$V_{ca} = V_{R_3} = R_3 \times I_{R_3} \quad I_{R_3} = 0$$

$$\Rightarrow V_{ab} = V_{cd} = V_s \frac{R_2}{R_1 + R_2}$$


step 3 Set $V_S = 0$

54

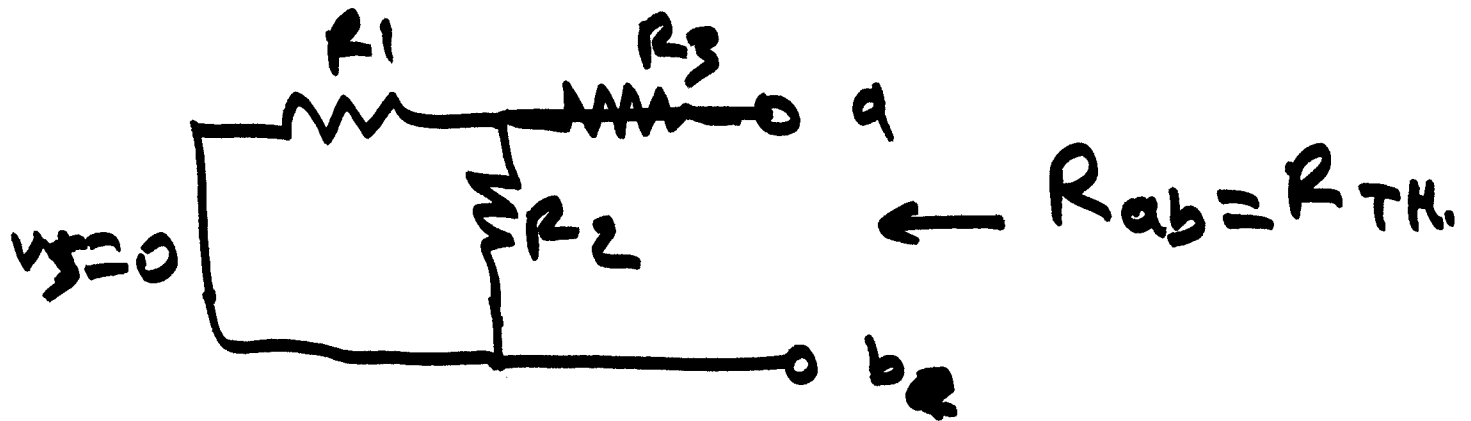

$$R_{ab} = R_{TH} = (R_1 || R_2) + R_3$$

Thevenin

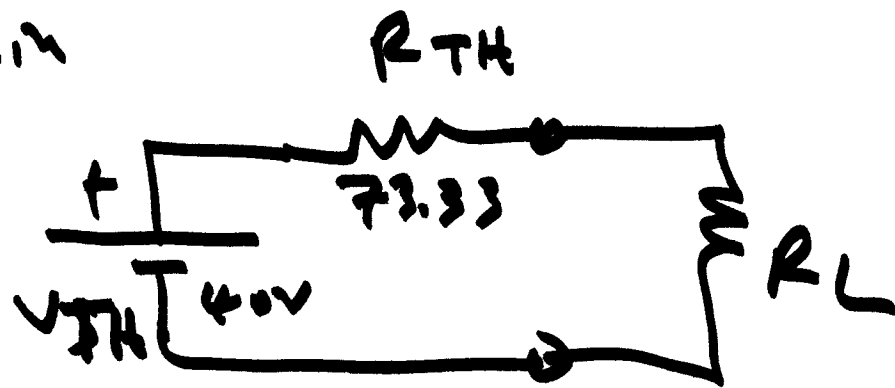


$$\Rightarrow V_{TH} = 120 \times \frac{20}{60} = 40V$$

$$R_{TH} = (20 || 40) + 60 = 73.33 \Omega$$

Theorem of maximum power transfer

55

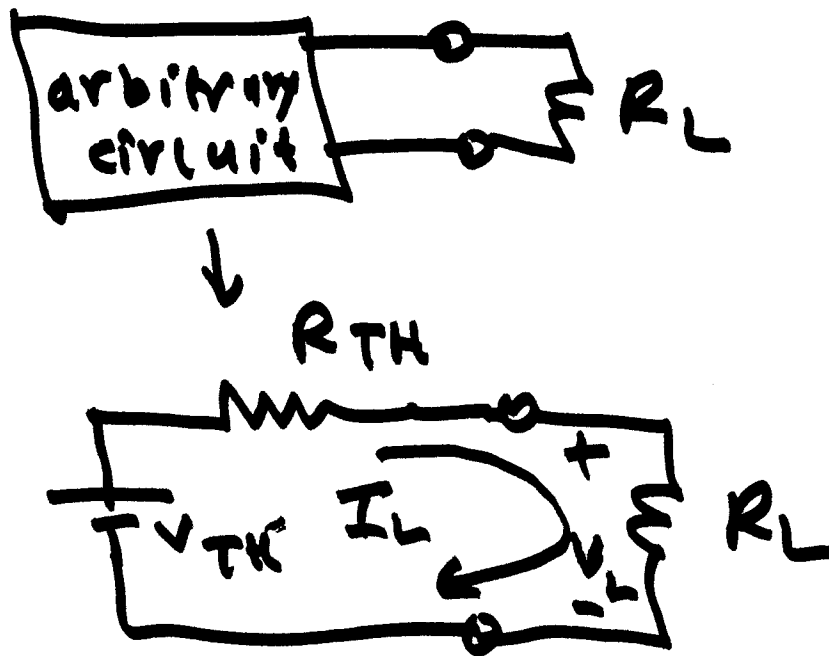

Find R_L for maximum power dissipation across R_L

P_L = power lost at R_L

$$P_L = I_L^2 R_L = \frac{V_L^2}{R_L}$$

$$I_L = \frac{V_{TH}}{R_{TH} + R_L}, \quad V_L = \frac{V_{TH} R_L}{R_L + R_{TH}}$$

$$P_L = V_{TH}^2 \cdot \frac{R_L}{(R_L + R_{TH})^2}$$

maximize

$$\frac{dP_L}{dR_L} = 0 \Rightarrow \dots V_{TH}^2 \frac{R_{TH} [\cancel{R_{TH}} - R_L]}{[R_{TH} + \cancel{R_L}]^3} = 0$$

$$\Rightarrow \boxed{R_L = R_{TH}}$$

Power is maximized
when $R_L = R_{TH}$

$$\frac{d^2 P_L}{dR_L^2} = V_{TH}^2 \left[\frac{-(R_{TH} + R_L)^3 - 3(R_{TH} - R_L)(R_{TH} + R_L)^2}{(R_{TH} + R_L)^6} \right]$$

$$\text{when } R_L = R_{TH} \Rightarrow \frac{d^2 P_L}{dR_L^2} < 0$$

maximum

what is the value
of the maximum power?

(57)

maximum when $R_L = R_{TH}$

$$\Rightarrow P_{L, \max} = V_{TH}^2 \frac{R_{TH}}{(R_{TH} + R_{TH})^2}$$

$$P_{L, \max} = \frac{V_{TH}^2}{4R_{TH}}$$


$$\text{Efficiency} = \frac{\text{Productive (useful)}}{\text{Total}}$$

In this case:

$$\text{Productive} = P_L$$

$$\text{Total} = \text{Delivered by Source}$$

Power delivered by
source

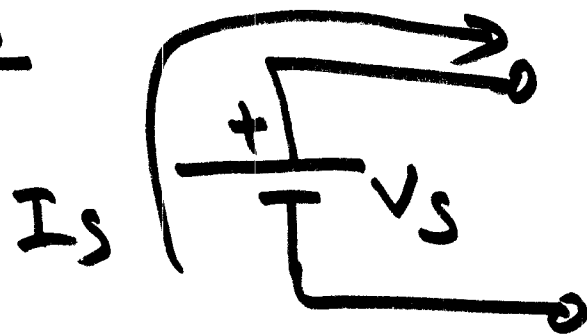

$$P_{\text{delivered}} = V_s \cdot I_s$$

In previous circuit

$$I_L = I_s = \frac{V_{TH}}{R_{TH} + R_L} = \frac{V_{TH}}{2R_{TH}}$$

$$R_L = R_{TH}$$

P_s = Power from source

$$P_s = V_{TH} \cdot I_L = \frac{V_{TH}^2}{2R_{TH}}$$

% efficiency, η

(59)

$$\eta = \frac{P_L}{P_S} \times 100\%$$

$$\Rightarrow \eta = \frac{\frac{V_{TH}^2}{4 R_{TH}}}{\frac{V_{TH}^2}{2 R_{TH}}} = \frac{1}{2} = 50\%$$

at maximum power

HW a) Find the value of R_L that maximizes the efficiency

b) Find the maximum R_{TH} efficiency

