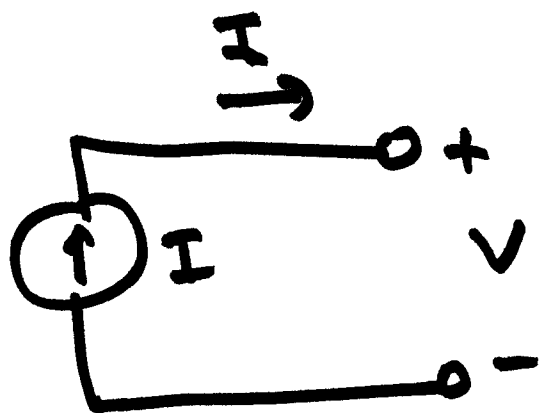


Ideal current source


(35)

1123/02



$$R_{eq} = \frac{\Delta V}{\Delta I}, \quad \Delta I = 0$$
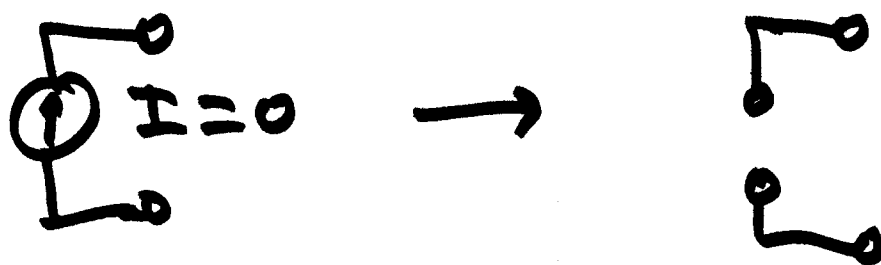
$$\Rightarrow R_{eq} \rightarrow \infty$$



Summary

set sources to zero

1) voltage \rightarrow short circuit


2) current \rightarrow open circuit



Independent vs. Dependent Source

- A) Independent: Voltage or current is fixed, set by the source
- B) Dependent: Voltage or current is not fixed, but it depends on something (another parameter)

Symbol notation

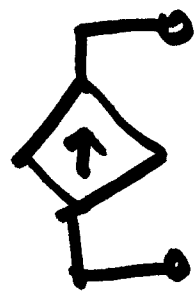

$k \cdot i$

$k \cdot i_A$

Dependent

current source

Superposition

(Theorem, Principle)

37

Linear function

$$y = f(x)$$

$x \rightarrow$ variable

$f(\cdot) \rightarrow$ function

$y \rightarrow$ result of x

$x_1, x_2 \rightarrow$ two different inputs

$$y_1 = f(x_1)$$

$$y_2 = f(x_2)$$

$$x_1 + x_2$$

$$y_3 = f(x_1 + x_2)$$

Example

$$x_1 = 10^\circ$$

$$x_2 = 20^\circ$$

$$f(\cdot) = \sin(\cdot)$$

$$y_1 = \sin(10^\circ)$$

$$y_2 = \sin(20^\circ)$$

$$y_3 = \sin(10+20) = \sin(30^\circ)$$

$$y_3 \neq y_1 + y_2$$

If function is Linear

(38)

then $y_3 = y_1 + y_2$

Example $y = \int x dx$

$$y_1 = \int x_1 dx$$

$$y_2 = \int x_2 dx$$

$$y_3 = \int (x_1 + x_2) dx$$

$$= \underbrace{\int x_1 dx}_{y_1} + \underbrace{\int x_2 dx}_{y_2}$$

$$\Rightarrow y_3 = y_1 + y_2$$

Definition of a Linear function

Linear if! a) $f(x_1 + x_2) = f(x_1) + f(x_2)$

and b) $f(kx) = k f(x)$


$k = \text{constant}$

or $f(k_1 x_1 + k_2 x_2) = k_1 f(x_1) + k_2 f(x_2)$

Simple test

(39)

$$y = f(x)$$

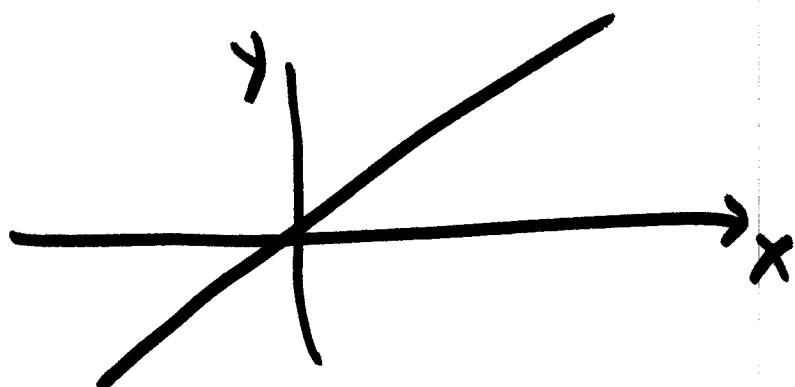

Linear if plot of y vs. x is a straight line passing through the origin




Example:

Resistor

Let

$$y = I$$


$$x = V$$

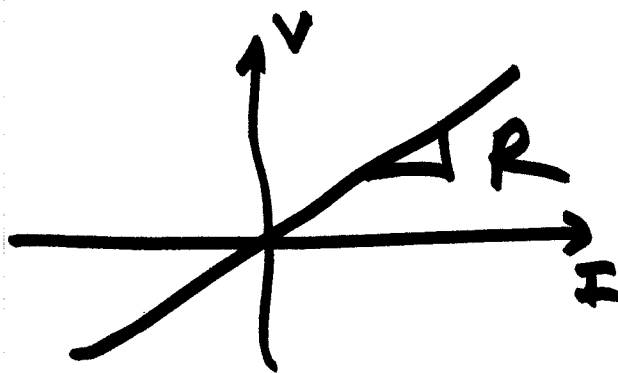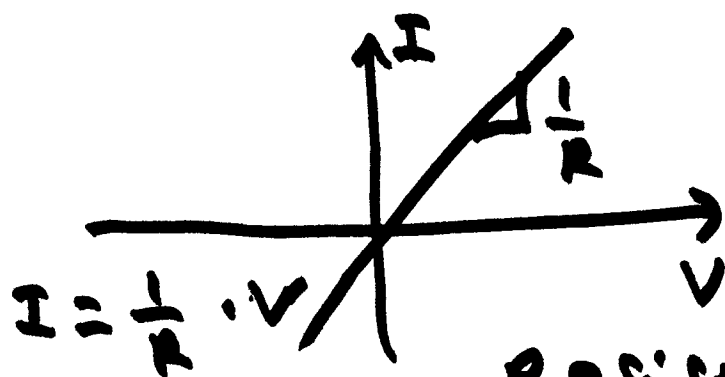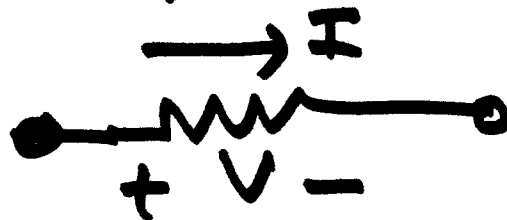

Resistor is a Linear component


Example 2

A diode

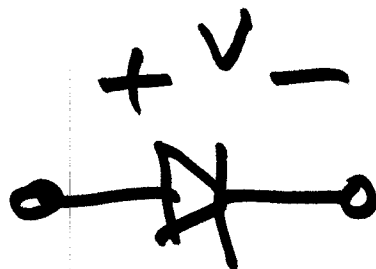

(40)

$$I = I_0 (e^{V/V_T} - 1)$$

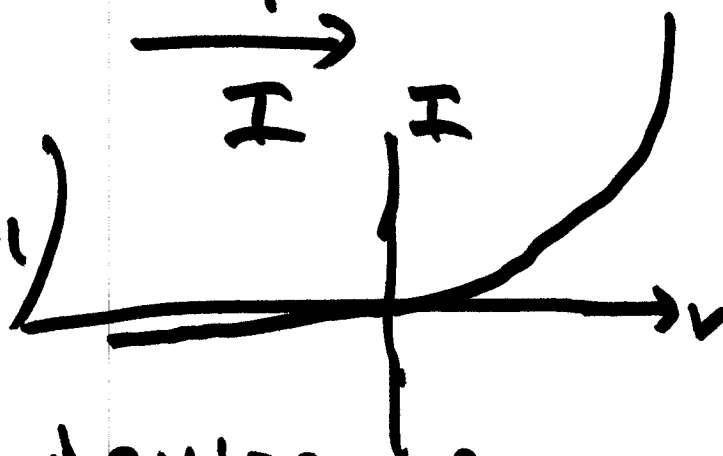

Non Linear device (component)

Circuits.

a) if a circuit is made up of Linear components, then the circuit is called Linear.

b) if a circuit contains at least one non-Linear component, then the circuit is non Linear.


So, In a Linear function (41)

$$y_1 = f(x_1)$$

$$y_2 = f(x_2)$$

$$\text{then } f(x_1 + x_2) = f(x_1) + f(x_2) \\ = y_1 + y_2$$

Superposition Capitalized
in circuits

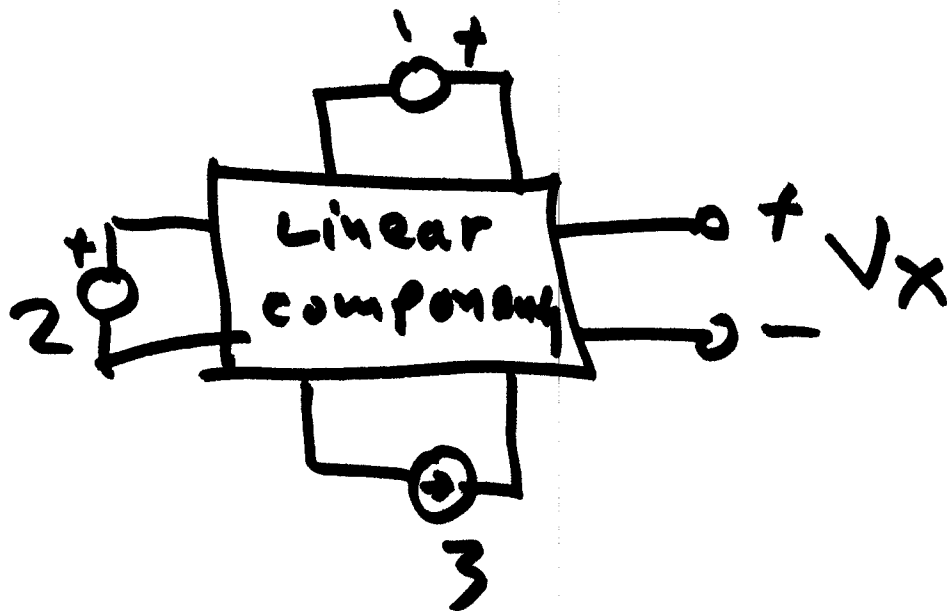

V_{x1}	voltage	due to Source 1
V_{x2}	"	" " " 2
V_{x3}	"	" " " 3

$$\Rightarrow V_x = V_{x1} + V_{x2} + V_{x3}$$

Superposition theorem


(42)

- 1) Assume Linear circuit
- 2) Multiple Sources (Inputs)
- 3) Compute an unknown (voltage or current) result of inputs.

Theorem The result of all inputs applied together, is equal to the summation of individual result of each input applied individually, with the rest set to zero

Example 1

(43)

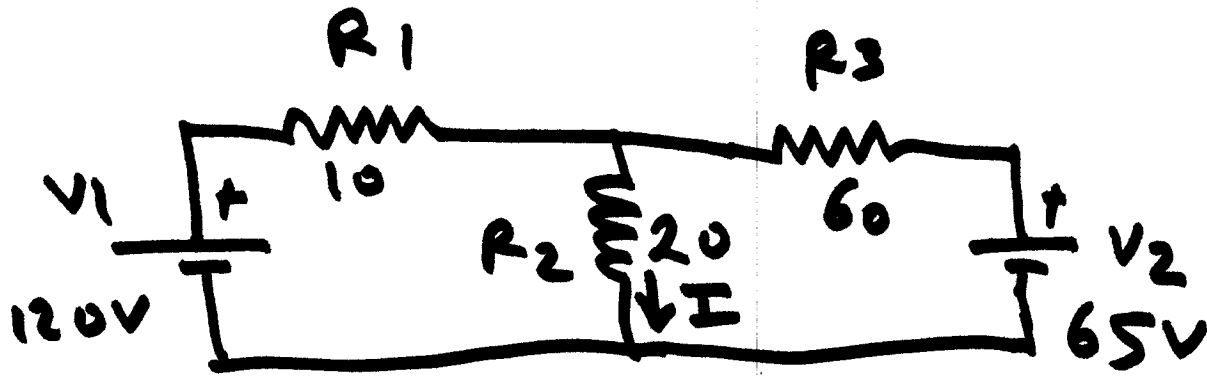


Find current I


use super position

First set

$$V_2 = 0$$

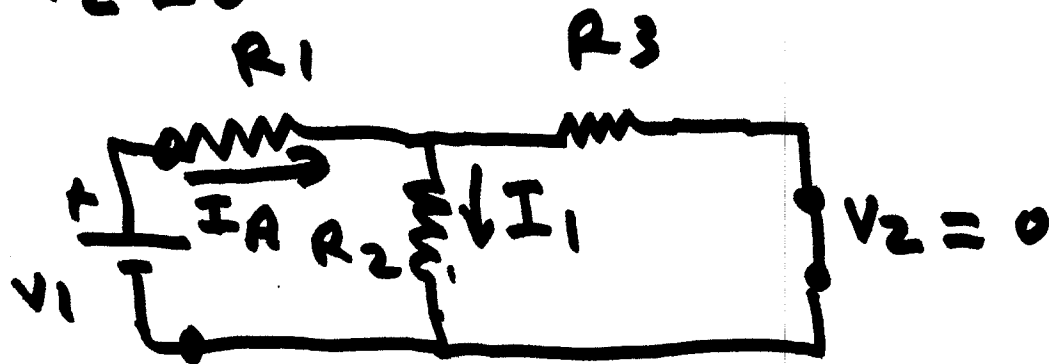

Then set $V_1 = 0$

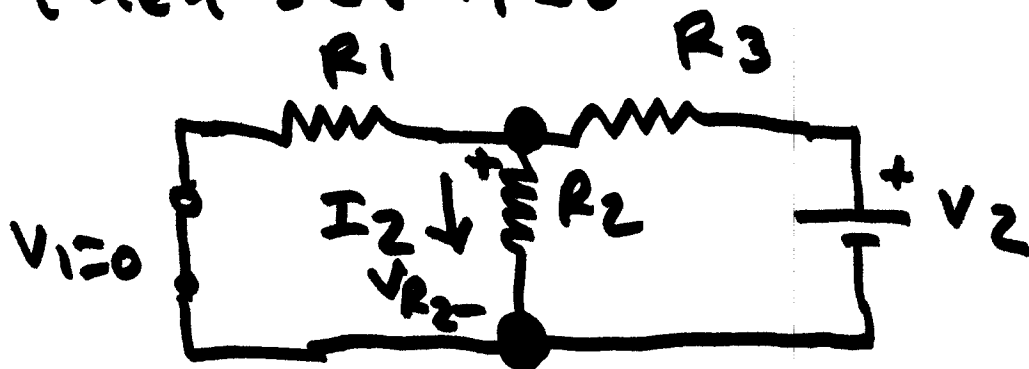

$$I = I_1 + I_2$$

Compute I_1 : use current divider

(44)

$$I_1 = I_A \frac{R_3}{R_2 + R_3}$$

$$I_A = \frac{V_1}{R_{eq}} \quad R_{eq} = R_1 + (R_2 \parallel R_3)$$


$$R_{eq} = 10 + (20 \parallel 60) = 10 + \frac{1200}{80} = 25 \Omega$$

$$I_A = \frac{120V}{25 \Omega} =$$

$$I_1 = \frac{120}{25} \frac{60}{80} = \cancel{1.6A} \quad 3.6A$$

$I_1 = 3.6A$

Find I_2 use voltage divider

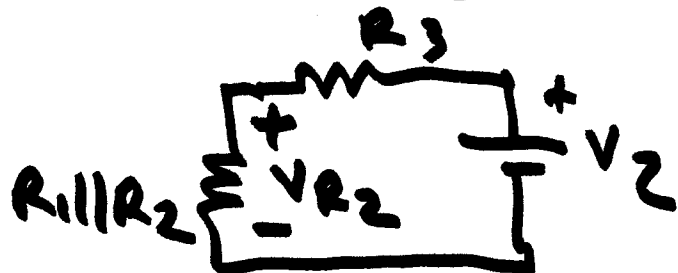

$$V_{R2} = V_2 \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_3}$$

$$V_{R2} = 6.5 \frac{6.66}{6.66 + 60} = 6.5V$$

$$\Rightarrow I_2 = \frac{V_{R_2}}{R_2} = \frac{6.5V}{20} = 0.325A$$

(4F)


$$I_1 = 3.6A, \quad I_2 = 0.325A$$

\Rightarrow Superposition


$$I = 3.6 + 0.325 = \underline{\underline{3.925A}}$$

Note: Superposition does not apply to power calculation because $P = V \cdot I$ is not a linear function

Example 2

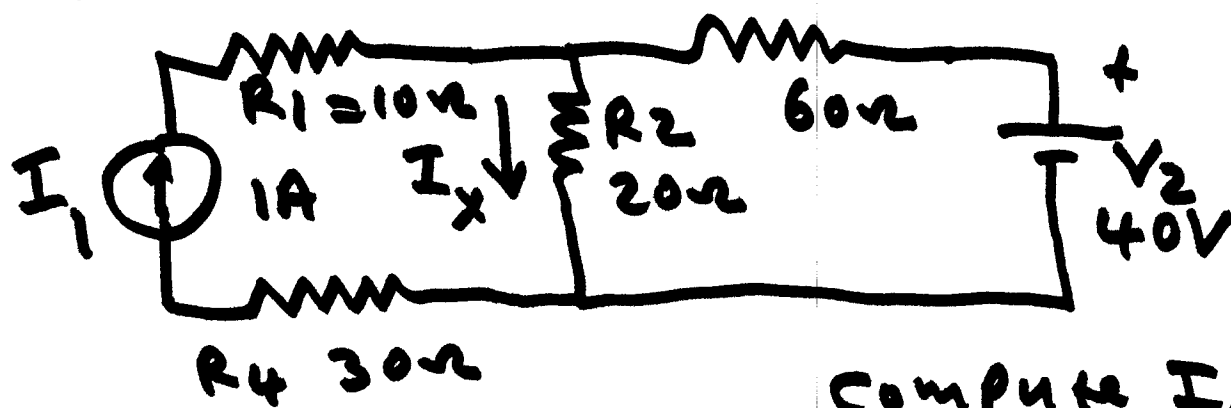


First consider the current source⁴⁶

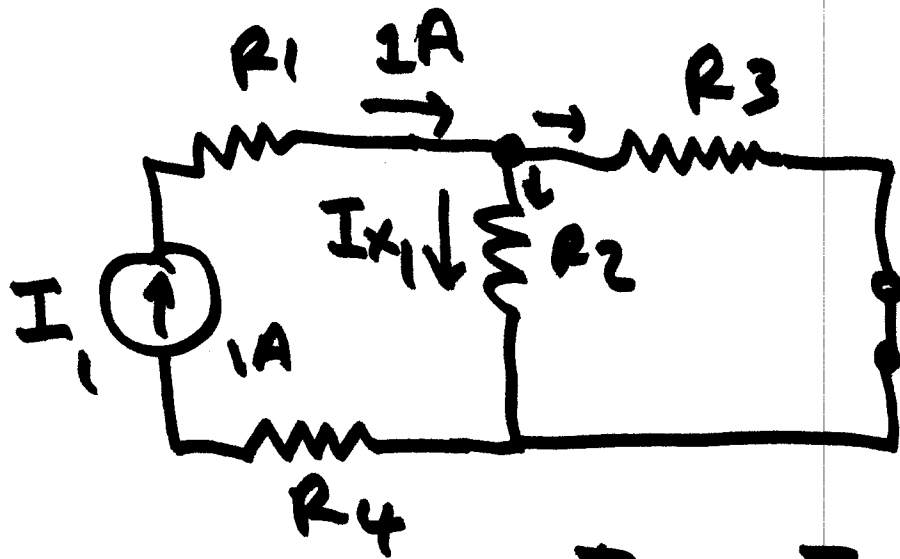

$$I_{x_1} = I_1 \frac{R_3}{R_2 + R_3}$$

$$= 1A \frac{60}{80} = \frac{3}{4} A$$

Next consider V_2

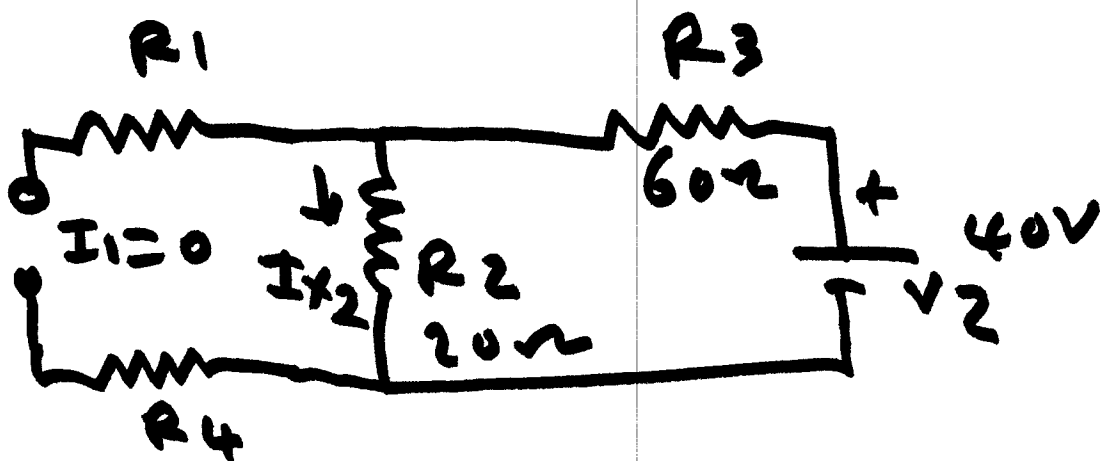

$$I_{x_2} = \frac{V_2}{R_{eq}} = \frac{40V}{80\Omega} = \frac{1}{2} A$$


$$\Rightarrow I_x = I_{x1} + I_{x2} = \frac{3}{4} + \frac{1}{2} = \underline{\underline{1.25 A}}$$

If the polarity of 40V source is reversed

$$\Rightarrow I_{x2} = -\frac{1}{2} A$$


$$\Rightarrow I_x = \frac{3}{4} - \frac{1}{2} = \underline{\underline{0.25 A}}$$

Definitions

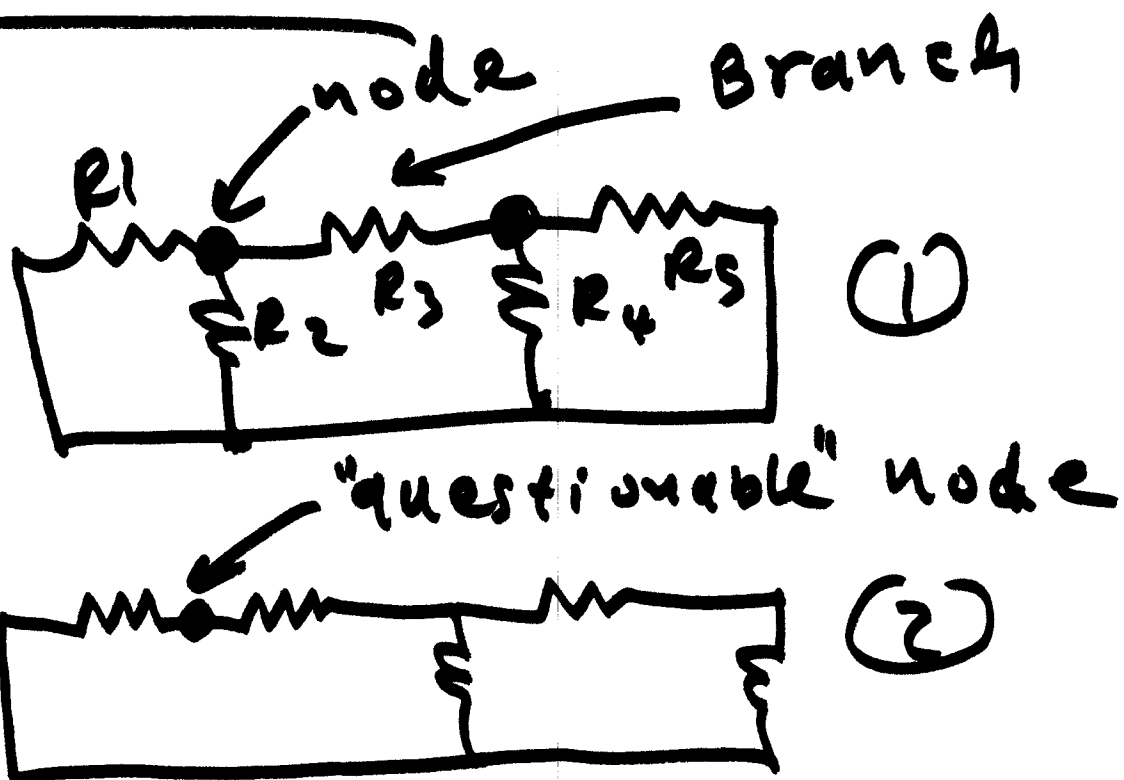

Re-draw #1

④

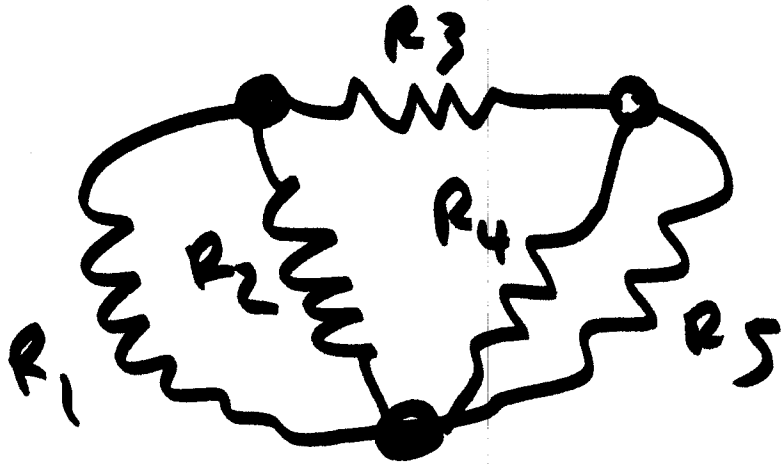

3 nodes