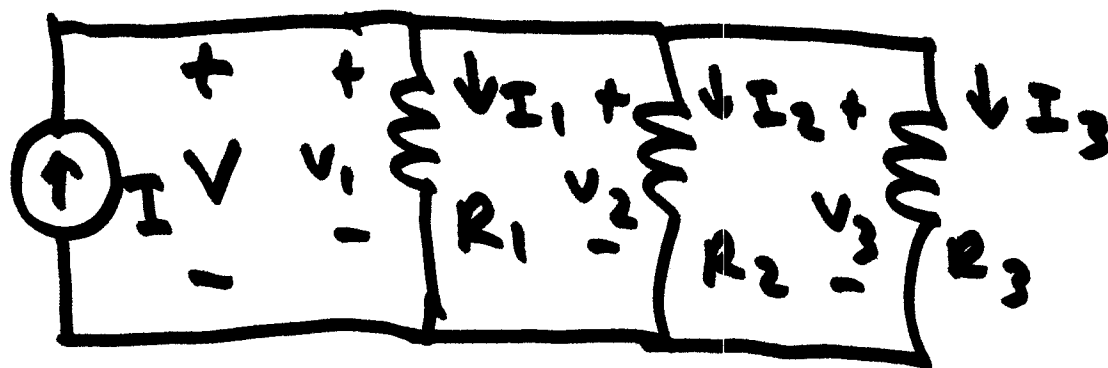


Example

(15)

1/14/02



You all agree that

$$V_1 = V_2 = V_3 = V$$

Since resistors are connected in parallel

$$\text{By KCL } I = I_1 + I_2 + I_3 \quad (A)$$

$$\text{By Ohm's Law } I_1 = \frac{V_1}{R_1} \quad \text{etc}$$

$$I_2 = \frac{V_2}{R_2}, \quad I_3 = \frac{V_3}{R_3}$$

$$(A) \Rightarrow I = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$I = V \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right]$$

$$V = I \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}} \quad (B)$$

(18)

$$I_1 = \frac{V}{R_1} = \frac{I}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

$$I_2 = \frac{V}{R_2}$$

$$I_3 = \frac{V}{R_3}$$

Question



From (B)

$$\underbrace{I \times \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}}_{\underbrace{\hspace{1.5cm}}} = \underbrace{I \cdot R_{eq}}_{\underbrace{\hspace{1.5cm}}}$$

$$\Rightarrow R_{eq} = \frac{1}{\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}}$$

or

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

Generalize for N Resistors

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \dots + \frac{1}{R_N} = \sum_{k=1}^N \frac{1}{R_k}$$

Resistors in Parallel

For two resistors

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$


$$\Rightarrow R_{eq} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

for 2 resistors

Back to example

18

How about 2 resistors only

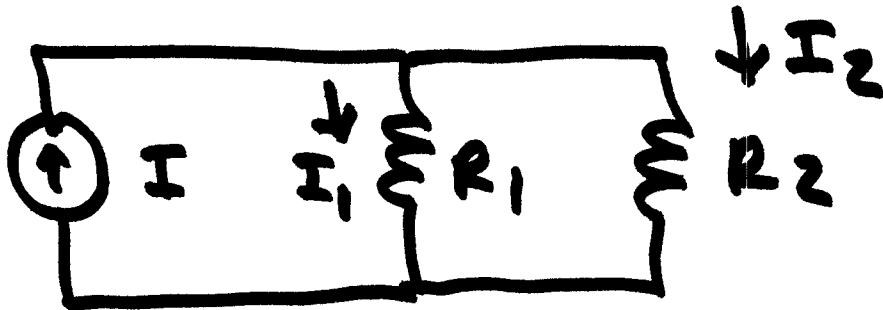

$$\text{Let } R_3 \rightarrow \infty$$

$$\Rightarrow I = \frac{V}{R_1} + \frac{V}{R_2} \Rightarrow V = I \left[\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}} \right]$$


$$I_2 = \frac{V}{R_2} = I \frac{\frac{1}{\frac{1}{R_1} + \frac{1}{R_2}}}{R_2}$$

$$I_2 = I \frac{1}{R_2 \left[\frac{1}{R_1} + \frac{1}{R_2} \right]}$$

$$I_2 = I \frac{1}{R_2 \left[\frac{R_1 + R_2}{R_1 \cdot R_2} \right]} = I \frac{R_1 R_2}{R_2 [R_1 + R_2]}$$

(19)

$$I_2 = I \frac{R_1}{R_1 + R_2}$$

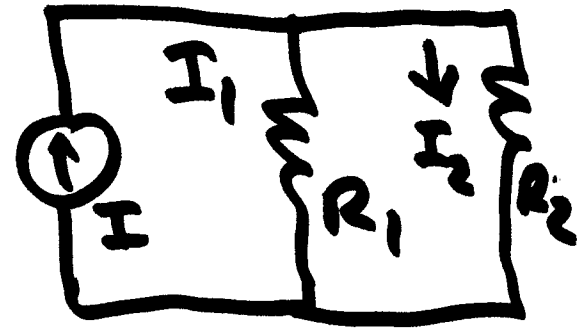


and

$$I_1 = I \frac{R_2}{R_1 + R_2}$$

Current divider

Example

Example 1

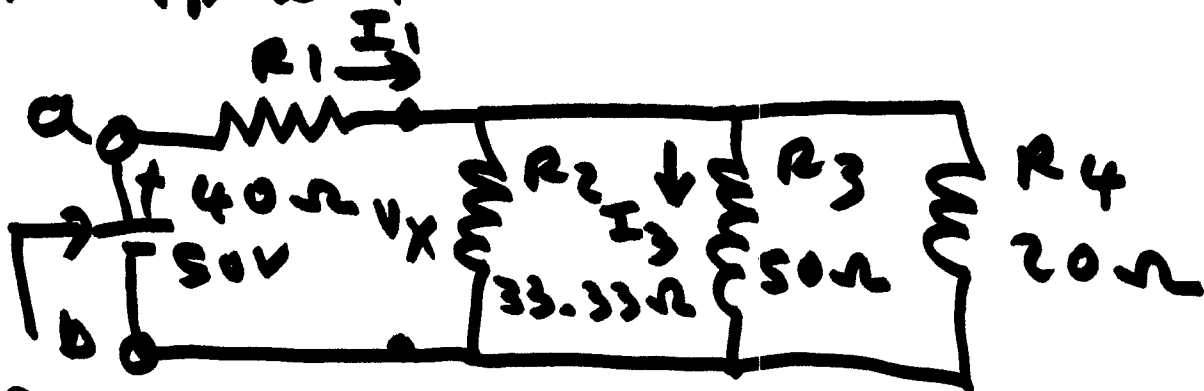

Req

Find Req between point a, b



$$\Rightarrow R_{eq} = R_1 + [R_2 || R_3 || R_4]$$

(20)

$$R_2 || R_3 || R_4 = \frac{1}{\frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_4}} = 10\Omega$$

$$\Rightarrow R_{eq} = 40\Omega + 10\Omega = \underline{\underline{50\Omega}}$$

expand example.

Compute current in R_3

if 50V source is connected

method 1 use voltage divider

$$V_x = 50V \frac{10\Omega}{10 + 40} = 10V$$



$$V_{R_3} = V_x \quad (\text{voltage across } R_3)$$

$$I_3 = \frac{V_x}{R_3} = \frac{10V}{50\Omega} = \underline{\underline{0.2A}}$$

method 2 use current divider

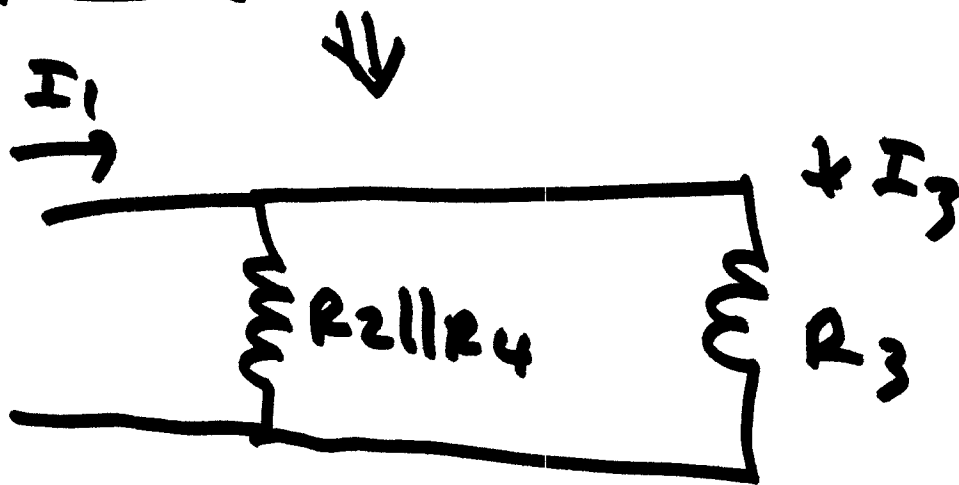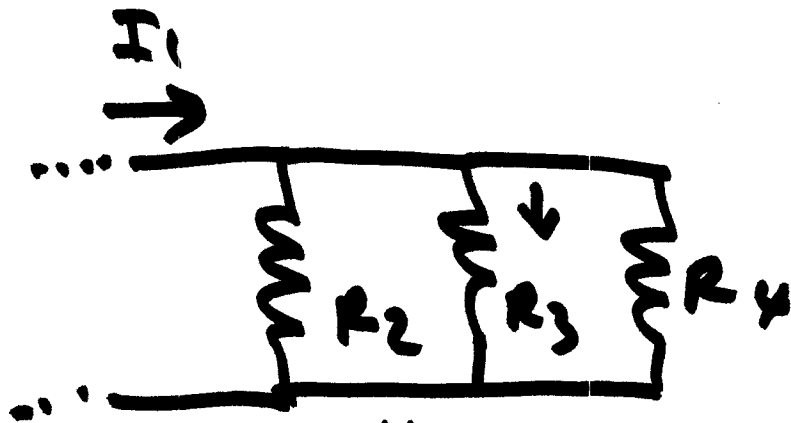(21)

$$I_1 = \frac{50V}{R_{eq}} = \frac{50V}{50\Omega} = 1A$$




$$I_3 = I_1 \frac{R_2 || R_4}{R_2 || R_4 + R_3}$$



$$R_2 || R_4 = \frac{R_2 \cdot R_4}{R_2 + R_4} = \frac{20 \times 33.33}{53.33} = 12.5\Omega$$

$$I_3 = 1A \frac{12.5}{12.5 + 50} = \frac{12.5}{62.5} = \underline{\underline{0.2A}} \quad (22)$$

Example 2

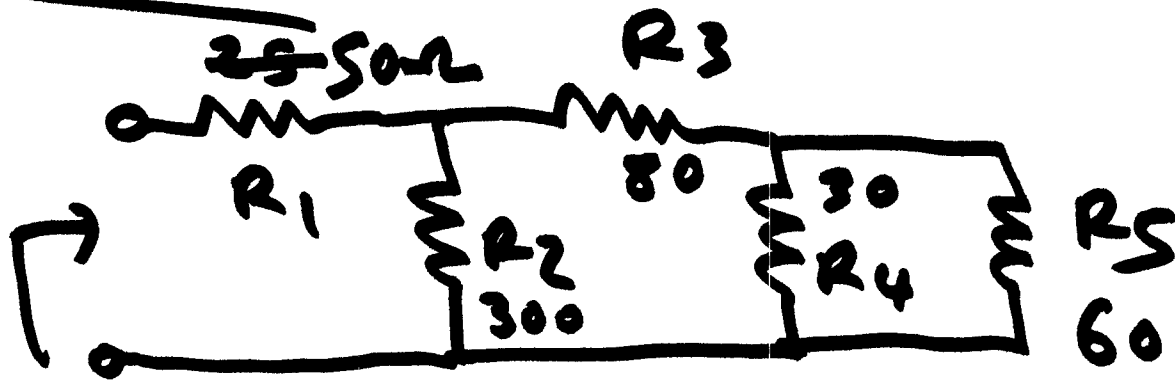

R_{eq}

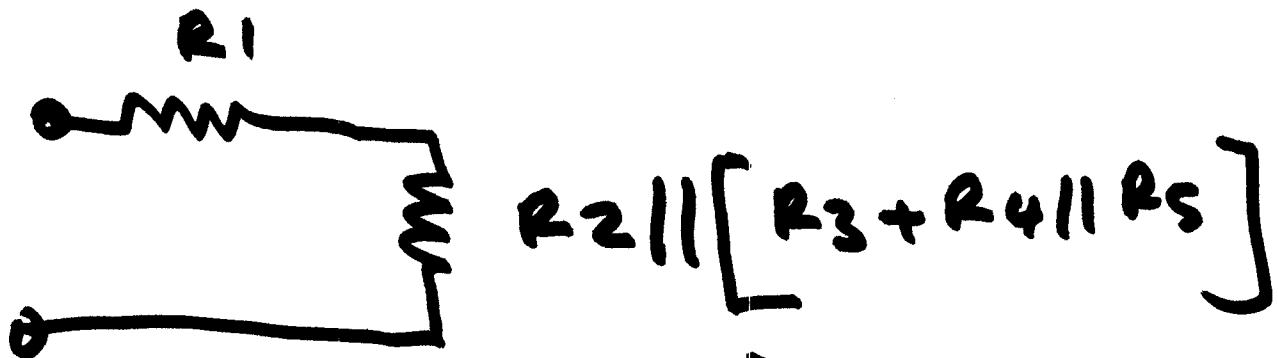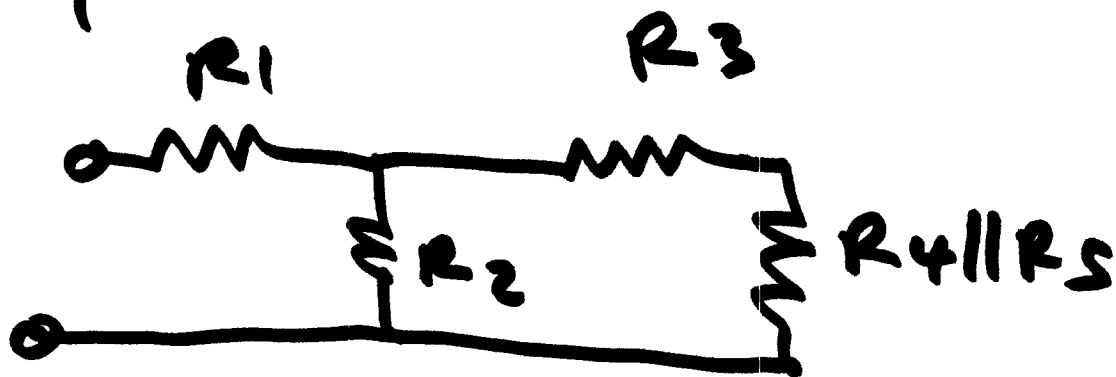

$$R_{eq} = R_1 + R_2 \parallel [R_3 + R_4 \parallel R_5]$$


$$R_4 \parallel R_5 = 30 \parallel 60 = 20$$

(23)

$$R_3 + R_4 \parallel R_5 = 80 + 20 = 100 \Omega$$

$$R_{eq} = \underbrace{25}_{50} + \underbrace{300 \parallel 100}_{75\Omega} = \underline{\underline{125\Omega}}$$

Example 3

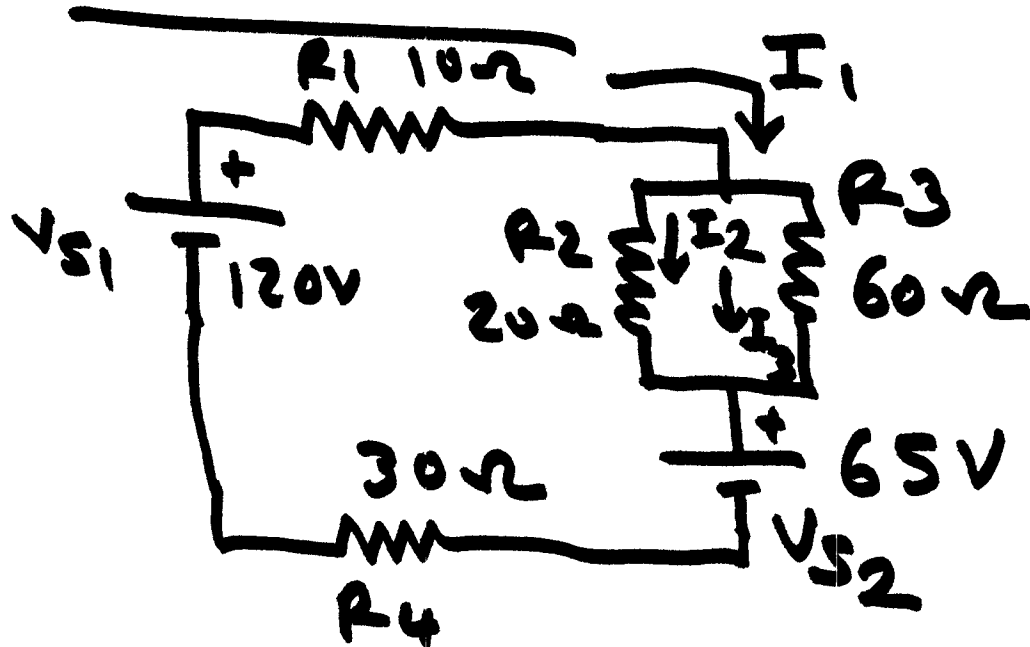

Find
 I_2, I_3

A method: Compute I_1 and
apply current
divider

For computing I_1 , combine
 $R_3 \parallel R_2$