

Jan 7. 02

6

Element used in Electrical Engineering

- 1) Passive : Resistors
capacitors (condensers)
Inductors (coils)
chokes
- 2) Active (Electronic components)
 - 1) transistors
 - 2) Diodes
 - 3) Operational Amplifiers
 - 4) Vacuum tubes

Lossy and lossless Components

Lossy:- Always dissipate energy (Resistor)

Lossless:- Do not dissipate energy
store energy (Capacitor
Inductor)

Time invariant vs. time variant

time invariant:- Physical properties
are constant in time

Resistors

(2)


Electrical symbol



R : Resistance in ohms (Ω)
($k\Omega$) 10^3
($M\Omega$) 10^6
($m\Omega$) 10^{-3}

Electric current: due to moving electron

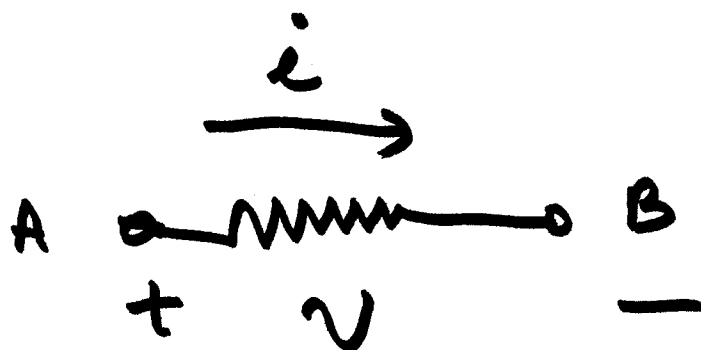
$$\left. \begin{array}{l} I : \text{Electric current} \\ i : \end{array} \right\} = \frac{dq}{dt}$$



V or \mathcal{V} : Voltage


③

4A 10^{-6} A

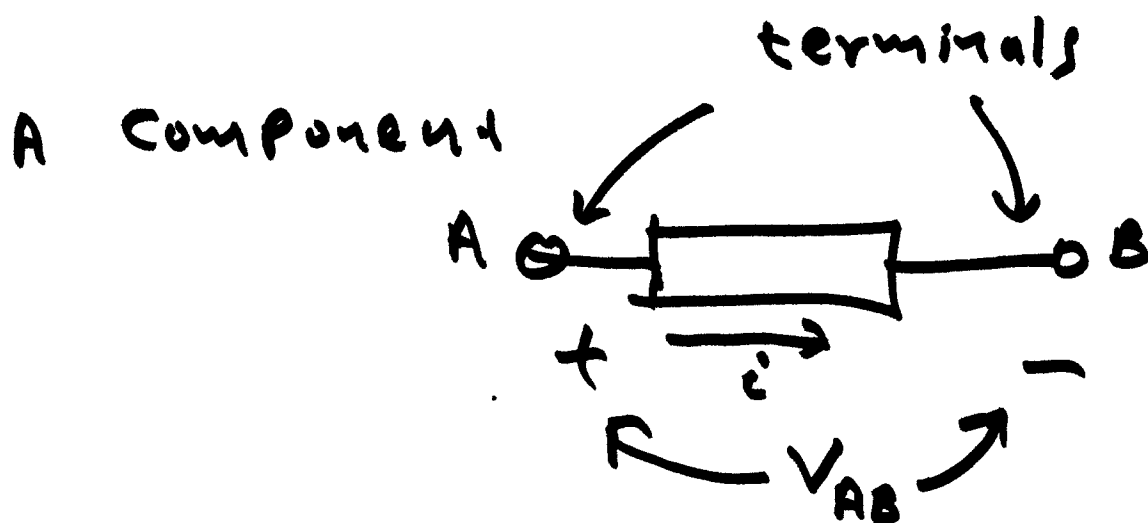[illegible]

Note: Voltage (or voltage difference) exists between two points (nodes)


voltage has a polarity

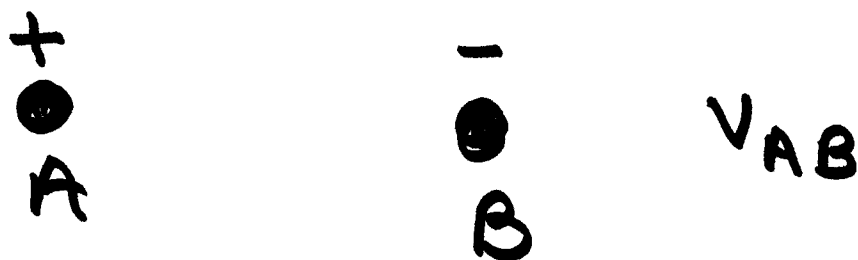


current flows in a branch (path)

current has a direction
(of flow)

(4)

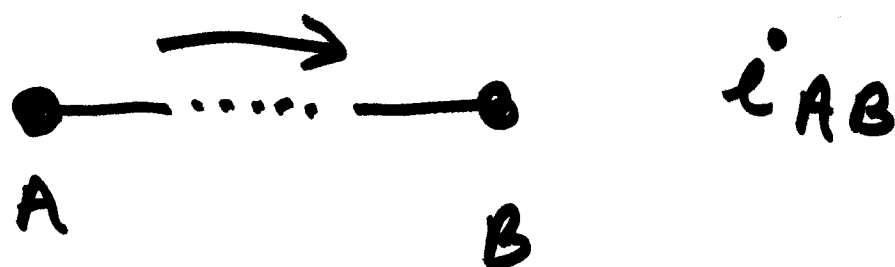


Back to the component

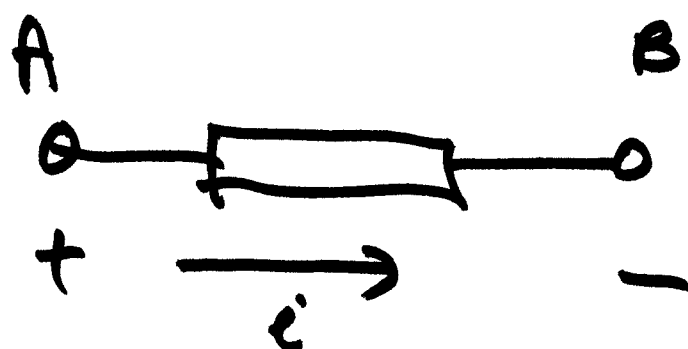

Lossy convention of polarity
and directions: Current flows
from + to - \Rightarrow energy
is dissipated.

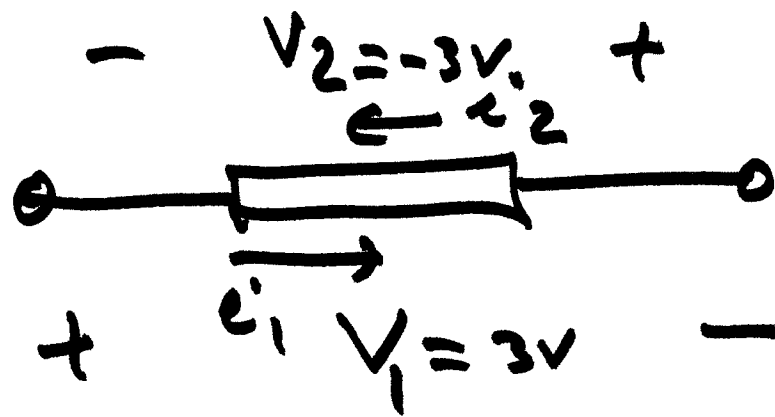Since a resistor is a lossy
element (component), the
current flows from + to -




(5)

$$V_1 = -V_2$$

$$i_1 = -i_2$$

Back to Resistor component

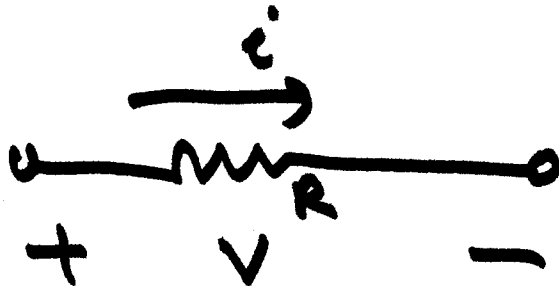

Relationship between V, i .
 Ohm had discovered that

$$i \sim V$$

$$\left. \begin{aligned} i &= \frac{V}{R} \\ V &= i \cdot R \end{aligned} \right\} \text{ohm's law}$$